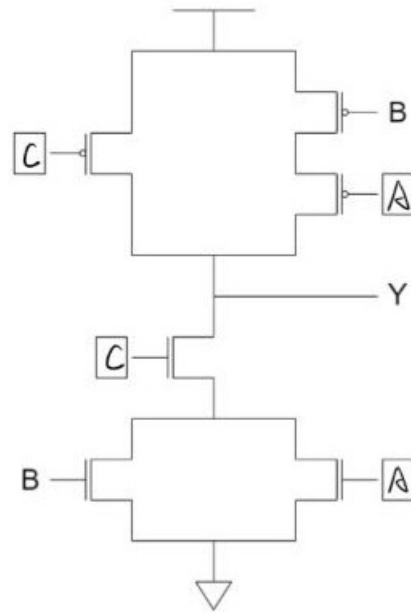


**T 1**

Truth Table			
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Figure 1: Circuit

**T 2****Prove:**

Simply prove that NOT AND OR can be represented by NAND:

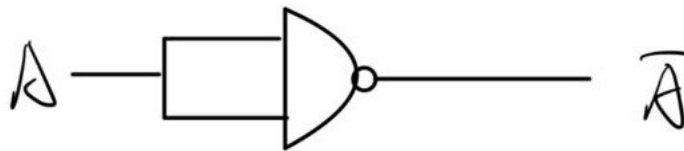
**Not**

Figure 2: NOT

AND

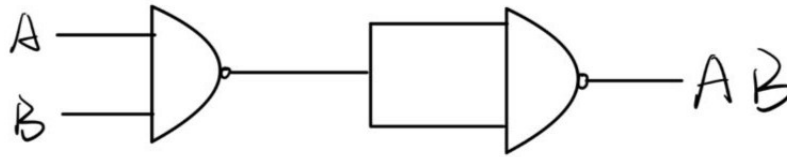


Figure 3: AND

OR

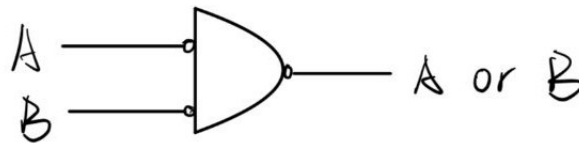


Figure 4: OR

In this way we have proved that NAND is logically complete.

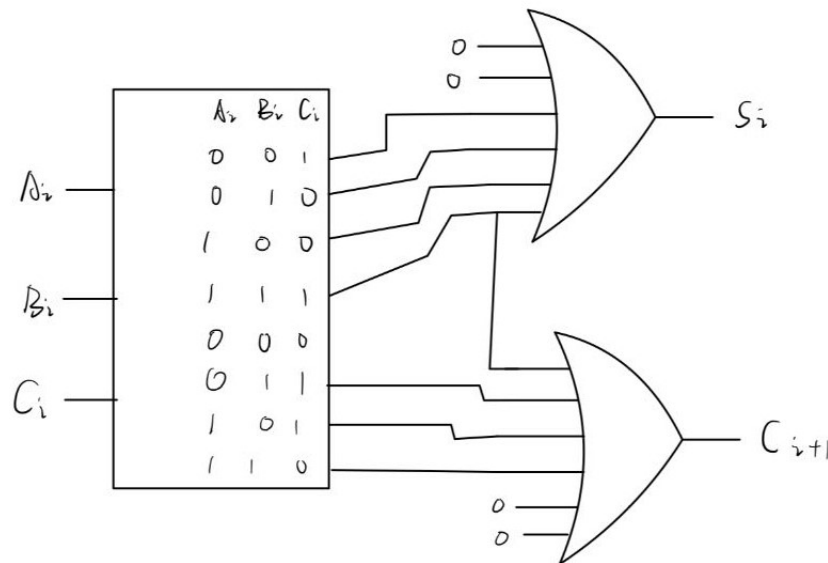
**T 3**

Figure 5: Full Adder


**T 4**

1. The maximum value of  $A[1:0]$  is 3(11).
2. The maximum value of  $B[1:0]$  is 3(11).
3. the maximum possible value of  $Y$  is 9(1001).
4. 4 bits.
5. As below

A[1]	A[0]	B[1]	B[0]	Y[3]	Y[2]	Y[1]	Y[0]
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

Table 1: Truth table

6. Implement the third bit of output,  $Y[2]$  from the truth table using only AND, OR, and NOT gates:

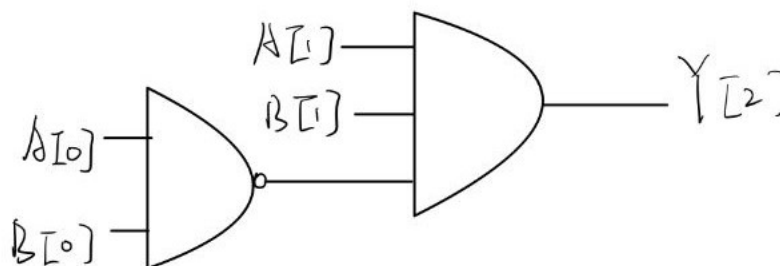Figure 6:  $Y[2]$

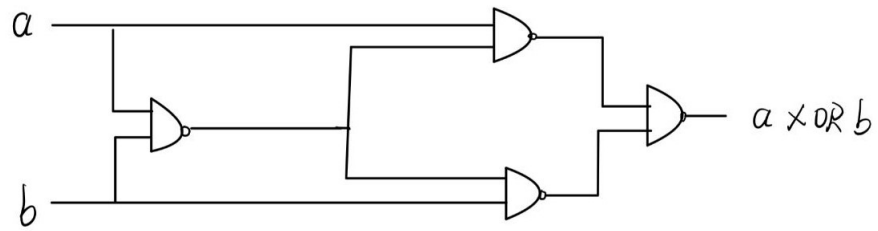
**T 5**

Figure 7: XOR

## T 6

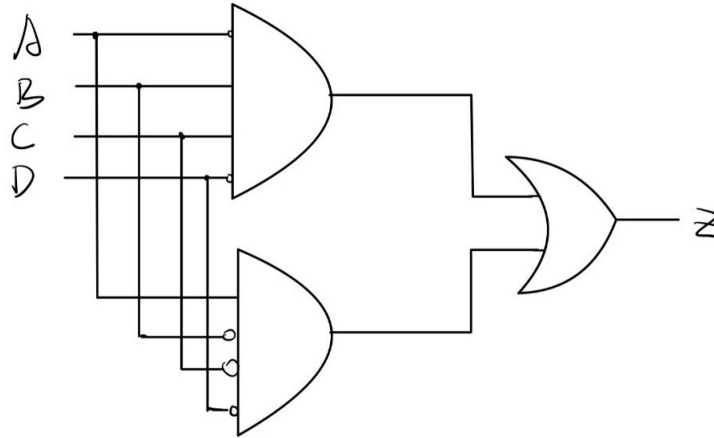


Figure 8: Logic circuit

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0

Table 2: Truth Table

**T 7**

1.

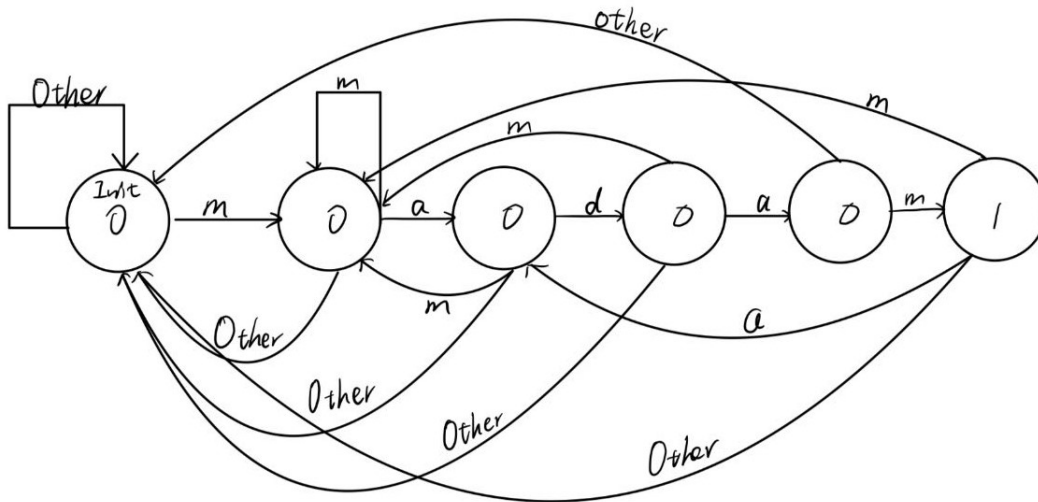


Figure 9: State diagram

2.

In this case, there are six unique states, so we would need a minimum of **six** latches to implement this FSM.

**T 8**

- The maximum address space of the memory is  $2^a$  addresses.
- the memory has an address space of  $2^a$  addresses, and each address can store B bits of data, so the total data capacity is  $2^a \cdot b$  bits.

**T 9**

- $A[1:0] = 00$  ;  $WE = 1$ .
- Just need to add k Gated D-Latches to each line and connect them as shown in the diagram.
- We need 6 line to find  $2^8 - 1$  address , so we need to add 4 lines.

**T 10****1. At least 82 bits**

- **occupation ratio** : Every team needs 7 bits , cause  $2^7$  is the smallest numbers that bigger than 99.
- **score** : Every team needs 2 bits.
- **time remaining** : 8 bits , 2 fot the minutes and 6 for the seconds.
- **skill charge ratio** : Every player needs 7 bits.

**2. Still 82****3. I'm sorry that I have no idea about this question.**